

Machine Structures 2 catch up exam solution

Exercise 1 : (4 points)

1. Digital electronics are electronics where logical values 0 and 1 are the main circuit signals. (1 point)

2. The truth table and the logical expression of a tristate buffer : (1 point)


A	C	S
0	0	Z
1	0	Z
0	1	0
1	1	1

logical expression :

$$\begin{cases} \text{if } (C=0) \Rightarrow S=Z \\ \text{if } (C=1) \Rightarrow S=A \end{cases}$$

3. The difference between synchronous and asynchronous sequential circuits, is that the synchronous keep track of the clock while executing. Whereas, the asynchronous don't. (1 point)

 4. The schematics of RS-Latch and its truth table : (1 point)





R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	Q'	\bar{Q}'
1	1	0	0

Exercise 2 : (5 points)


Case A = 0 and B = 0 : (1 point)

Case : A = 0 and B = 0

  


Case A = 1 and B = 0 : (1 point)

Case : A = 1 and B = 0

 


Case A = 0 and B = 1 : (1 point)

Case : A = 0 and B = 1

 

Case A = 1 and B = 1 : (1 point)

Case : A = 1 and B = 1

 

The circuit truth table : (0,5 point)

A	B	Q	
0	0	Q'	Memorize
0	1	0	Reset to 0
1	0	1	Set to 1
1	1	0	Reset to 0


This asynchronous sequential circuit could be used as RS-Latch (A as Set and B as Reset) (0,5 point)

Note : Despite the case A=1, B=1 is a reset, the circuit is still an RS-Latch. Because the case (1,1) is not supposed to be used in an RS-Latch.

Exercise 3 : (5 points)

1. Mux 2-1 Multiplexer :

Step 1 : Global Scheme (0,5 point)

 

Step 2 : Truth Table (0,5 point)

E0	E1	S	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Step 3 : Canonical Disjunctive Functions (0,5 point)


$$\text{Output}(E0,E1,S) = \bar{E0} \cdot \bar{E1} \cdot S + E0 \cdot \bar{E1} \cdot \bar{S} + E0 \cdot E1 \cdot \bar{S} + E0 \cdot E1 \cdot S$$

Step 4 : Karnaugh Map (0,5 point)


		E0E1			
	S	00	01	11	10
	0	0	0	1	1
	1	0	1	1	0

$$\text{Output}(E0,E1,S) = E0 \cdot \bar{S} + E1 \cdot S$$


Step 5 : Schematics (1 point)

 

2. Mux 4-1 Multiplexer : (1 point)

 


3. Mux 3-1 Multiplexer : (1 point)

 

Note : Putting only E3 to Z is not a valid solution. Because circuits don't behave normally with a Z value in their entries.


Exercise 4 : (6 + 1 bonus point)

Step 1 : Global Scheme (1 point)

 

U : for UP
 D : for DOWN
 M : for Motor

Step 2 : F.S.M. (1 point)

 

Step 3 : Transition Table (1 point)

Current State	U	D	Next State
S0	0	0	S0
S0	0	1	S0
S0	1	0	S1
S0	1	1	S0
S1	0	0	S1
S1	0	1	S0
S1	1	0	S1
S1	1	1	S1

Step 4 : Encoded States Table and Outputs Table (1 point)

State	S	M
S0	0	0
S1	1	1

Step 5 : Table de Transition Encodée (1 point)

S	U	D	S'
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Step 6 : Logical Functions (1 point)

$M(S) = S$ (directly deducted)

D \ SU	SU			
	00	01	11	10
00	0	1	1	1
01	0	0	1	0

$$S'(S,U,D) = U \cdot \bar{D} + S \cdot \bar{D} + S \cdot U$$

Step 7 : Schematics (1 point)

